



QUESTION WORKBOOK

# Resonant circuits and filters

Electronics · Year 13

AQA 3.13.3.1

17 questions · 51 marks

NAVY SCREEN EDITION

**SECTION A** · Warm-up

**A1** State how the reactance of an inductor and of a capacitor each change as the frequency rises, and state what happens at resonance in a series LC circuit. [2]

---

---

---

**A2** Define the Q factor of a resonant circuit, and state the unit in which it is quoted. [2]

---

---

---

**A3** A series LC circuit with resistance is driven by a variable-frequency source. State where the output must be taken to give a band-pass response and where to give a band-stop response. [2]

---

---

---

**A4** A resistor and a capacitor are connected in series across a signal source. State which component the output is taken across for a low-pass filter and which for a high-pass filter. [2]

---

---

---

**A5** Define the cut-off frequency of an RC filter, and state the output there as a fraction of the full output. [2]

---

---

---

**A6** State the effect of adding resistance to a tuned circuit on its resonant frequency, on the height of its resonance peak and on its bandwidth. [2]

---

---

---

---

## SECTION B · Standard

**B1** A tuned circuit is built from an inductor of 1.0 mH and a capacitor of 100 nF. Calculate its resonant frequency. [3]

- B2** A tuned circuit resonates at 15.9 kHz and has a Q factor of 10. Calculate its bandwidth and give the range of frequencies it passes. [3]

- B3** A series circuit of 1.0 mH and 100 nF, resonating at 15.9 kHz, has a total resistance of 25  $\Omega$ . Using  $Q = 2\pi f_0 L/R$ , calculate the Q factor and the bandwidth. [3]

- B4** A filter is made from a 1.6 k $\Omega$  resistor in series with a 0.10  $\mu$ F capacitor. Calculate its cut-off frequency. [3]

- B5** A low-pass filter is to have a cut-off frequency of 2.5 kHz using a 4.7 k $\Omega$  resistor. Calculate the capacitance required, and state which component the output is taken across. [3]

- B6** A radio's tuned circuit uses a fixed 1.0 mH inductor with a variable capacitor adjustable from 40 pF to 360 pF. Calculate the resonant frequency at each end of the range, and state the ratio of highest to lowest frequency. [3]

- B7** A measured resonance curve peaks at 40.0 kHz, and the current has fallen to  $1/\sqrt{2}$  of its peak value at 38.4 kHz and at 41.6 kHz. Calculate the bandwidth and the Q factor. [2]

## SECTION C · Stretch

- C1** A receiver's tuned circuit is centred on 200 kHz and must pass a signal 8.0 kHz wide, so its bandwidth may not be less than 8.0 kHz. The only inductor available is 250  $\mu\text{H}$ . Calculate the capacitance needed, the largest Q factor the circuit may have, and the smallest total circuit resistance that is acceptable, using  $Q = 2\pi f_0 L/R$ . Comment on what would go wrong if the resistance were made very much smaller. [7]

- C2** Speech occupying 300 Hz upwards shares a line with 50 Hz mains hum. A filter built from a 22 k $\Omega$  resistor is to have a cut-off frequency of 120 Hz. State which type of filter is needed, calculate the capacitance, and estimate the fraction of the hum that survives, given that a high-pass filter's output fraction is  $(f/f_c)/\sqrt{1 + (f/f_c)^2}$ . [4]

- C3** An audio line is to have 50 Hz mains hum removed by a band-stop filter built from an inductor in series with a  $1.0 \mu\text{F}$  capacitor. Calculate the inductance required, comment on whether the component is practical, and state where the output of the filter must be taken. [4]

- C4** Medium-wave stations are spaced 9 kHz apart. A receiver is tuned to a station on 909 kHz and its designer has wound the tuned circuit to a Q factor of 300. Calculate the bandwidth this gives, state the Q the receiver should have instead, and explain what the listener would hear with the Q of 300. [4]